



## Si825X FREQUENCY COMPENSATION SIMULATOR FOR DIGITAL BUCK CONVERTERS

### Relevant Devices

This application note applies to the Si8250/1/2 Digital Power Controller and Silicon Laboratories Single-phase POL Reference Design.

### 1. Introduction

The Frequency Compensation Simulator (FCS) enables the user to easily design and optimize closed-loop frequency compensation for buck converters based on the Silicon Labs Si8250 digital power controller. The FCS simulates both the controller and power stages providing a single simulation of the entire system. The intuitive user interface generates frequency response gain and phase graphs, and automatically generates filter coefficient values for the Si8250 in both decimal and hex formats.

### 2. Features

- System compensation design and optimization in a single intuitive simulation environment.
- Directly generates compensation loop filter coefficients for the Si8250 digital controller.
- Greatly reduces design and system verification time.

### 3. User Interface

The default FCS GUIs are shown in Figures 1 and 2. The Bode Plot GUI of Figure 1 illustrates the closed-loop magnitude and phase response for the Si8250-based buck converter. This GUI displays the response plots with loop bandwidth, and gain and phase margin data in real time, and includes a cursor function to facilitate plot measurement at any point. The Real Time Compensation data entry GUI shown in Figure 2 consists of multiple user interfaces, each with its own selection tab (the Setup GUI is shown). The user specifies power stage and controller parameters using this set of GUIs. (For example: power stage parameters such as output filter L and C values; Si8250 control parameters such as ADC LSB size and sampling frequency, PWM frequency, etc).

 


Figure 1. Default Bode Plot GUI

## 3.1. Setup GUI

The Setup GUI of Figure 2 allows the user to specify the top-level configuration of the system to be simulated. The Power Stage block represents the power circuits of a single or multiphase buck converter. The Delay block represents the unit delay (nS) through the power stages due to driver propagation delay and other factors. The Gain block (immediately following the Delay block) represents additional gain due to an external amplifier or other gain source. Each of these three blocks can be included in the simulation by "checking" (left mouse button click) the associated selection box. The remaining blocks in this GUI are related to the Si8250 digital controller. The selection shown in Figure 2 is typical, and consists of the ADC, PID and 2-pole low-pass filter, and DPWM modulator. The user can select any combination of blocks to be included (or excluded) from the simulation.

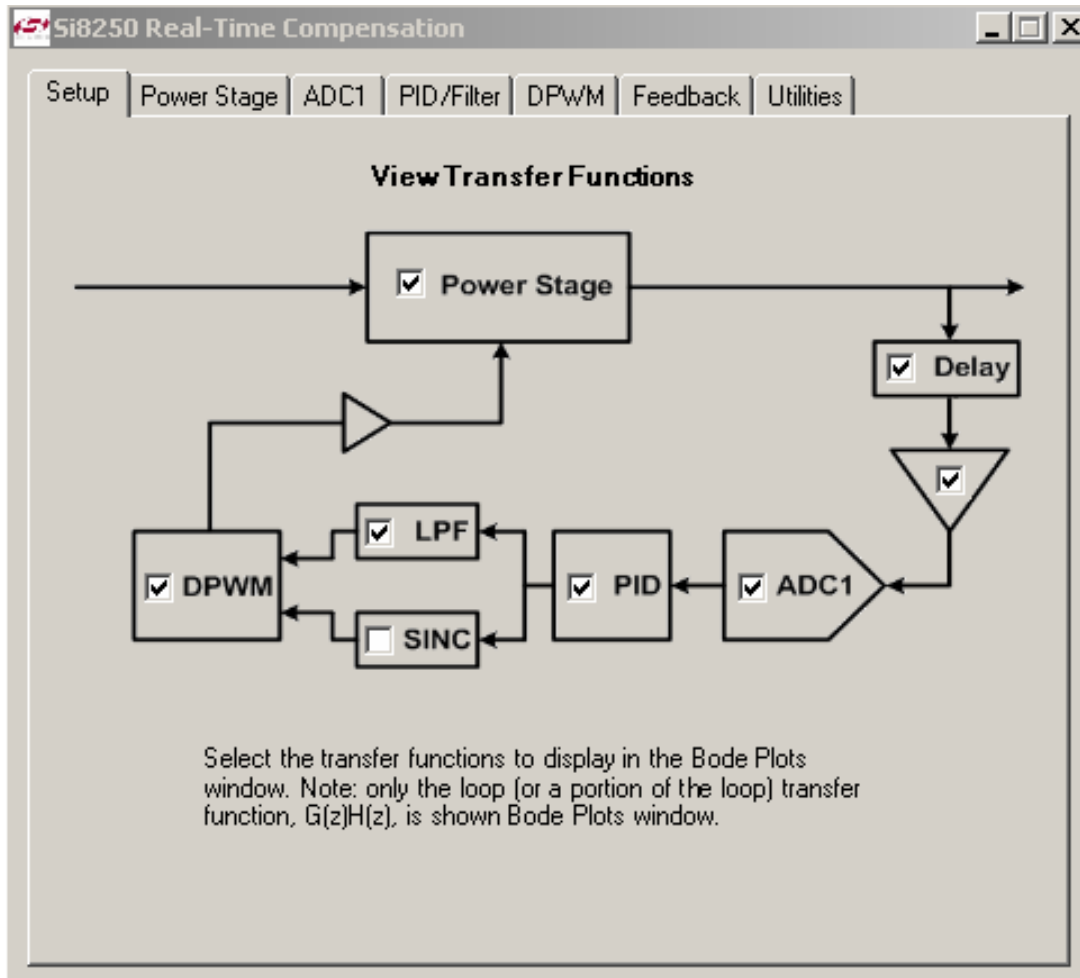


Figure 2. Default Setup GUI

### 3.2. Power Stage GUI

The Power Stage GUI (Figure 3) shows a single-phase buck topology. The user enters values for the converter input voltage ( $V_{in}$ ), the filter components (inductor and associated series resistance, capacitor and associated series resistance), and the output load resistance value. The up/down buttons associated with each field allow the user to increment or decrement the specified values by simply clicking on the appropriate button. As with all other GUIs in this tool, the specified values may also be changed by simply typing over them, then pressing the ENTER key. Although a single-phase schematic is shown, a multiphase circuit can be modeled by adjusting only the inductor parameters. For instance, an equivalent two-phase design would include two equally sized inductors whose values are one-half that of a single-phase design. To model this, both the inductor's DCR and L values need to be adjusted accordingly. All other parameters in the model remain the same.

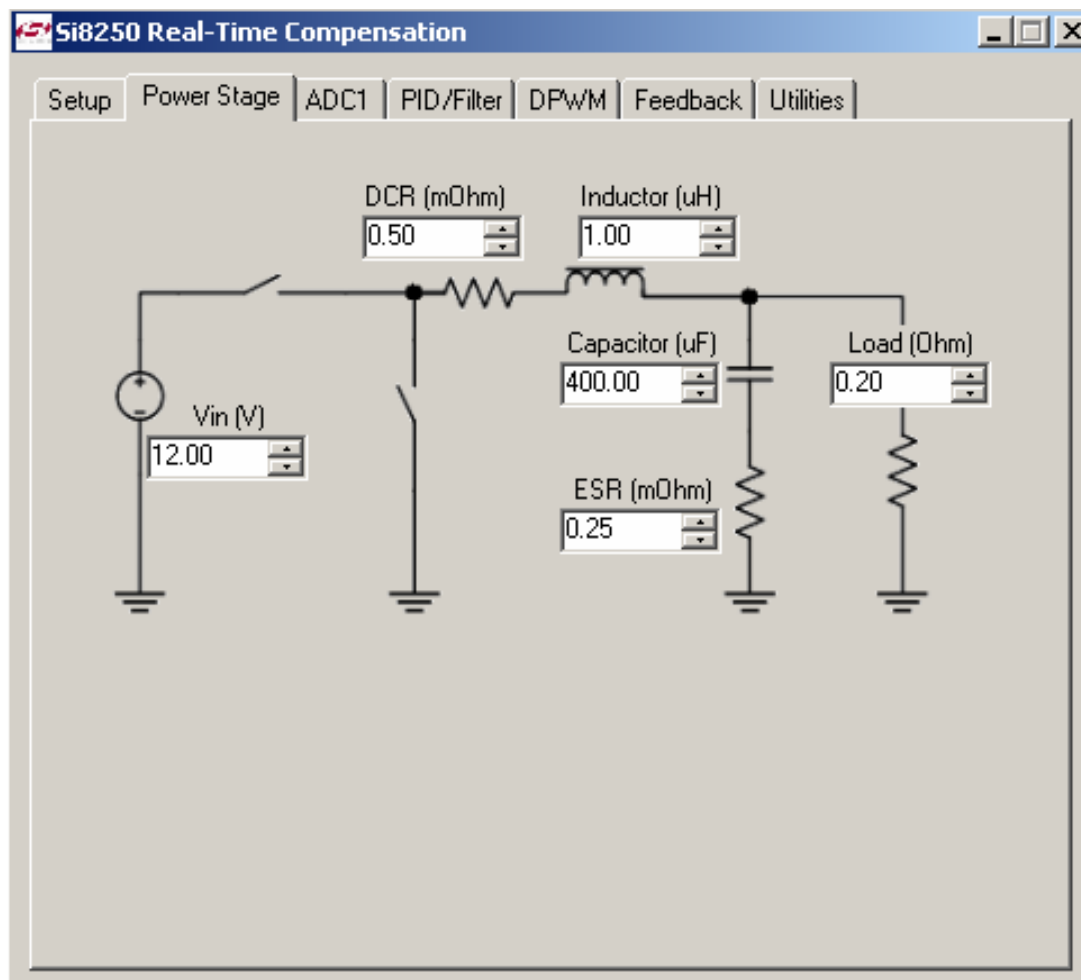


Figure 3. Power Stage GUI

# AN294

## 3.3. ADC1 GUI

The ADC1 GUI (Figure 4) allows the user to specify the sampling rate (in MHz) and the LSB size (in mV). For information on the operation of ADC1, please refer to the ADC1 chapter of the Si8250 Users Manual.

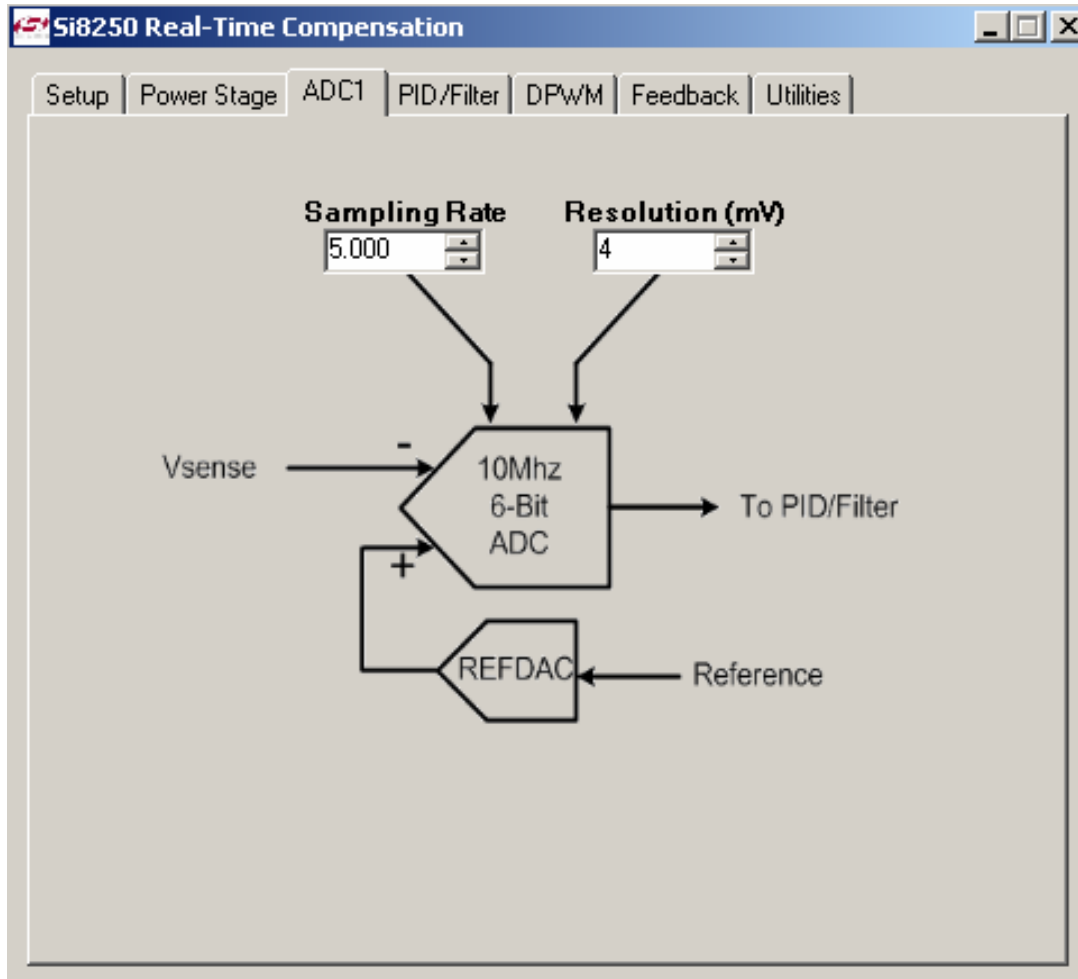


Figure 4. ADC1 GUI

### 3.4. PID/Filter GUI

The PID/Filter GUI (GUI) contains a group of slider controls allowing adjustment of the Si8250 loop compensation filter coefficients. (For more details on these parameters, please see the "DSP Filter Engine" chapter of the Si825x User Manual.) The default values in this GUI are for the Silicon Laboratories single-phase POL reference design, which is detailed in the "Appendix—Single-phase POL Reference Design Specifications" on page 17 of this document. After editing the power stage parameters to match the system to be simulated, the user typically maintains the default filter coefficient values as a starting point, and adjusts the sliders one at a time while observing the response on the Bode Plot display GUI until the desired frequency response is achieved. An example design exercise appears in "5. Using the FCS" on page 11.

 


Figure 5. PID/Filter GUI

## 3.5. DPWM GUI

The Si8250 contains a digital PWM modulator (DPWM) the output of which moves in discrete time steps. The maximum number of time steps for any given switching cycle is 511. The SW\_CYC field in the DPWM GUI (Figure 6) allows the user to specify the number of DPWM time steps per switching cycle. (For more information on DPWM operation, please see the DPWM chapter of the Si8250 Users Manual.)

 


Figure 6. DPWM GUI

### 3.6. Feedback GUI

The Feedback GUI (Figure 7) allows the user to specify values for the feedback divider resistors, and the capacitance seen by the resulting feedback voltage (which will typically include the anti-aliasing capacitor required for ADC1). The user must also specify any external gain (such as an external amplifier) and the power stage group delay (propagation delay of the gate drivers plus turn-on delay of the transistors, plus other external sources of delay) for maximum simulation accuracy.

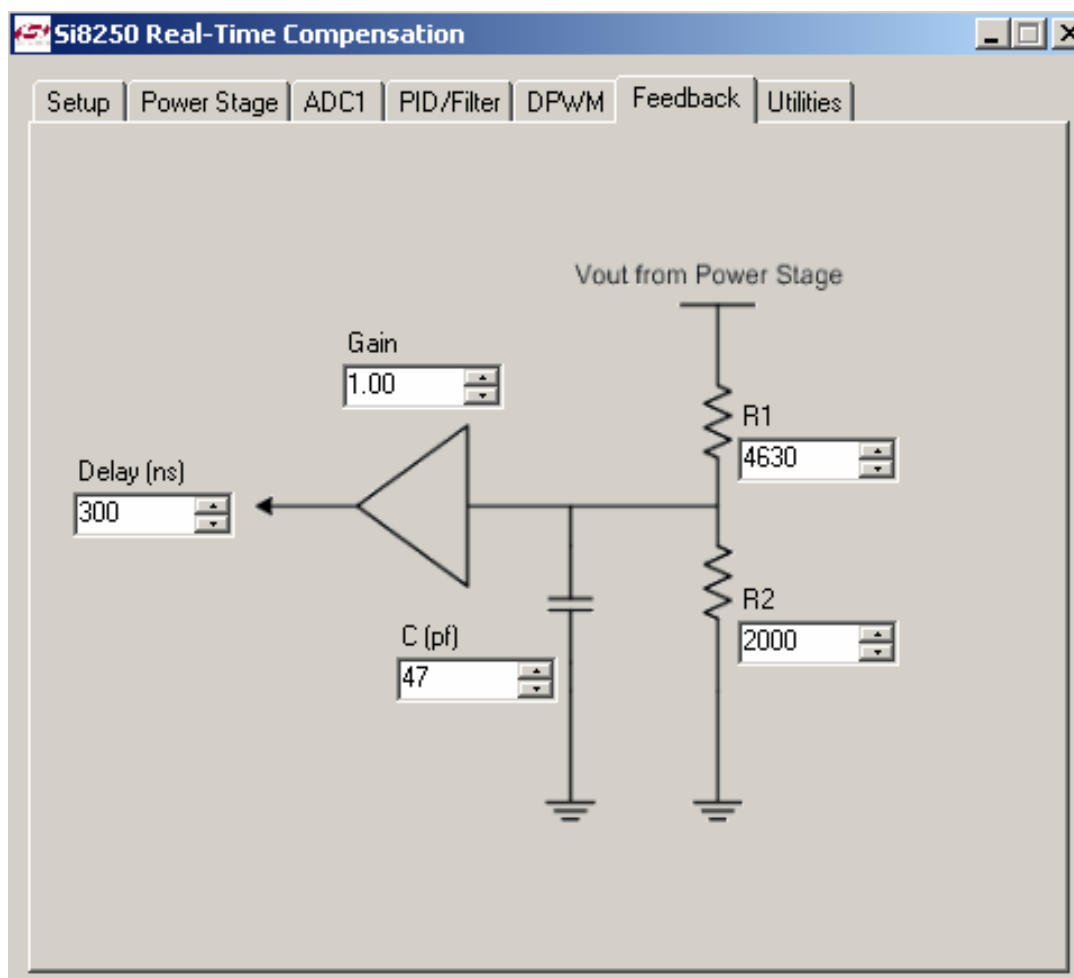


Figure 7. Feedback GUI

## 3.7. Utilities GUI

The Utilities GUI (Figure 8) provides the means to adjust the scale of the frequency plots that appear in the Bode Plot GUI. For instance, modifying the Gain Plot Scale button from 1 to 2 increases the amplitude of the plot in the Bode Plot GUI by 2. The Gain Plot Offset button shifts the Gain Plot up or down. This can be very useful when skewing sections of the plot for more detailed information. The Line Smoothing box eliminates digital sampling artifacts in the Bode Plot GUI for clearer viewing. The Sensitivity button increases the resolution of the Bode Plot GUI. When checked, the Enable Trace automatically updates the Freq, Phase, and Gain parameters at the top left of the Bode Plot display as the mouse is dragged over any portion plot for precise parameter measurement.


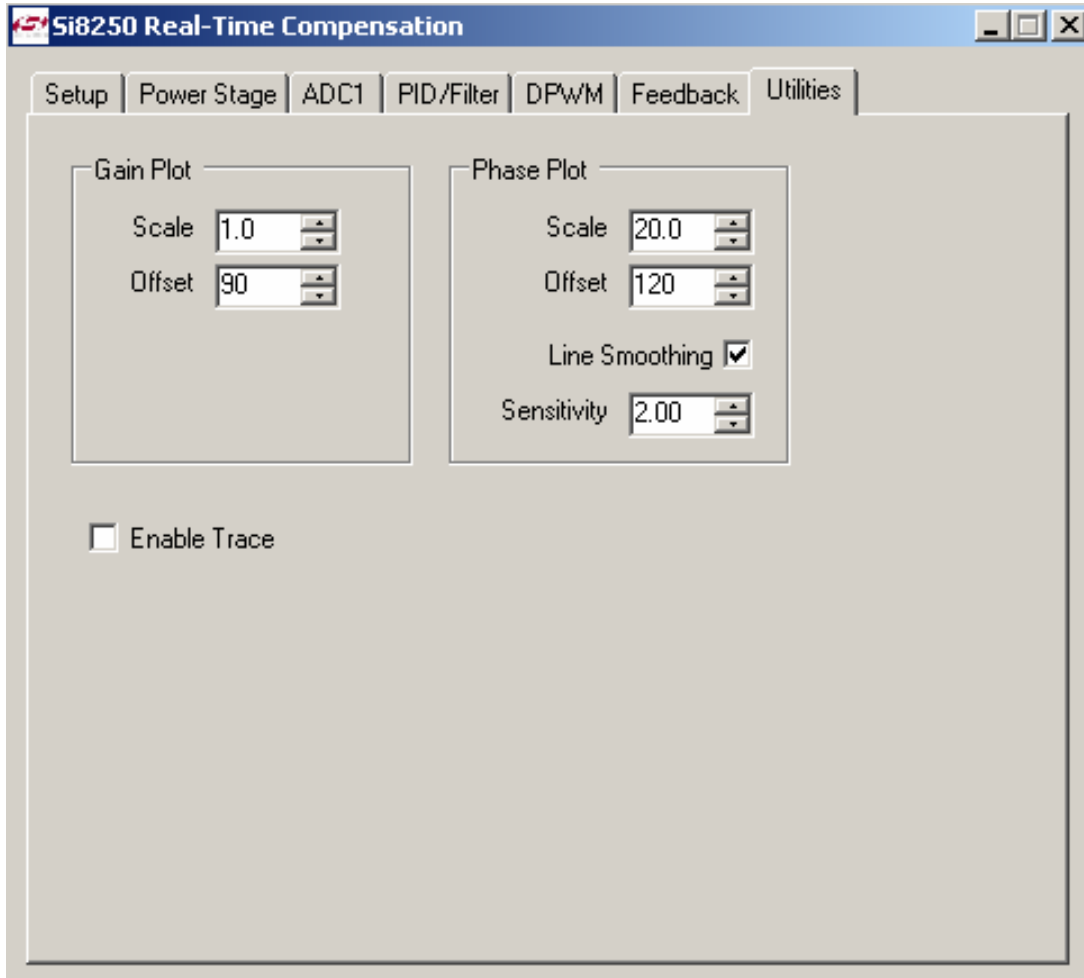


Figure 8. Utilities GUI

 

## 4. Cursors and Zooming

Cursors allow precise gain and phase margin measurements as shown in Figure 9. Gain and phase margin values at the cursor location are displayed in the upper left of the screen.



**Figure 9. Using Cursors and Zooming**

Zooming provides greater display resolution, and is accomplished by moving the mouse to the top left corner of the area to be zoomed, then clicking and dragging the mouse to the bottom right corner of the desired zoom area. A dotted box appears over the zoom area of interest (Figure 10). Once the area is chosen, release the left mouse button and the area will be zoomed. Note that multiple zooms into an area can be implemented. To return to the original non-zoomed Bode Plot GUI, click the left mouse button anywhere in the Bode Plot GUI.

 
 


Figure 10. Zooming

## 5. Using the FCS

This design example illustrates usage of the FCS, and is based on Silicon Labs' single-phase POL reference design board (detailed in "Appendix—Single-phase POL Reference Design Specifications" on page 17). The following parameters are repeated here for convenience:

- Input voltage: 12 V<sub>DC</sub>
- Output voltage: 3.3 V<sub>DC</sub> @ 20 A max
- Switching frequency: 380 kHz ±2%
- Output inductor: 1 H ±20% (DCR: 1.56 mΩ)
- Output caps: 410 F ±20% (Capacitor ESR: 1.25 mΩ)
- RDS(on): 2.5 mΩ

The desired frequency response is:

- Loop Bandwidth: 35 kHz
- Phase margin: 45 deg

### 5.1. Configuring the GUIs

Launch the FCS and edit the data in each GUI to match the settings shown in Figures 11–16.

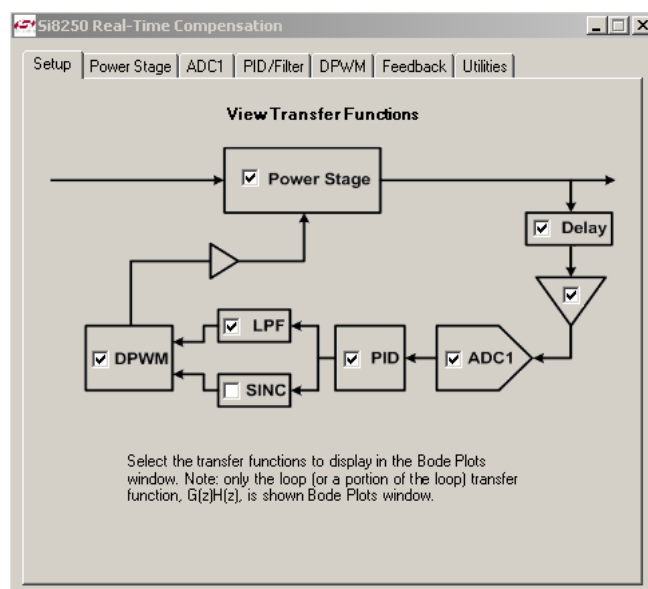


Figure 11. Set-up GUI

 


Figure 12. Power Stage GUI

 


Figure 13. ADC1 GUI

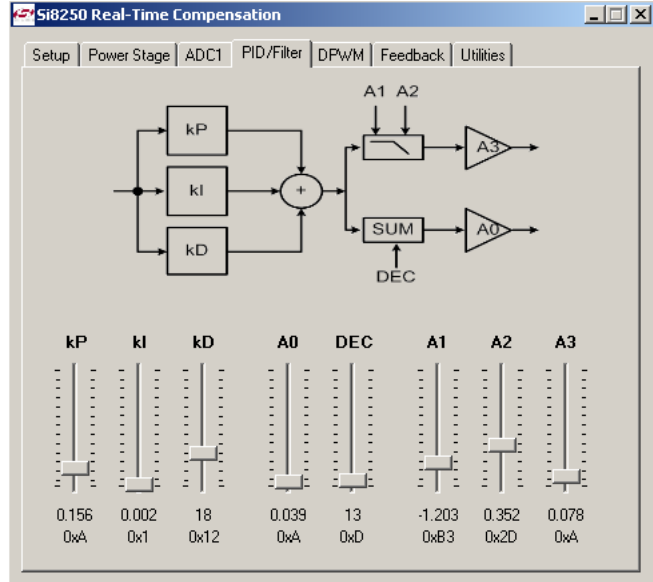


Figure 14. PID/Filter GUI

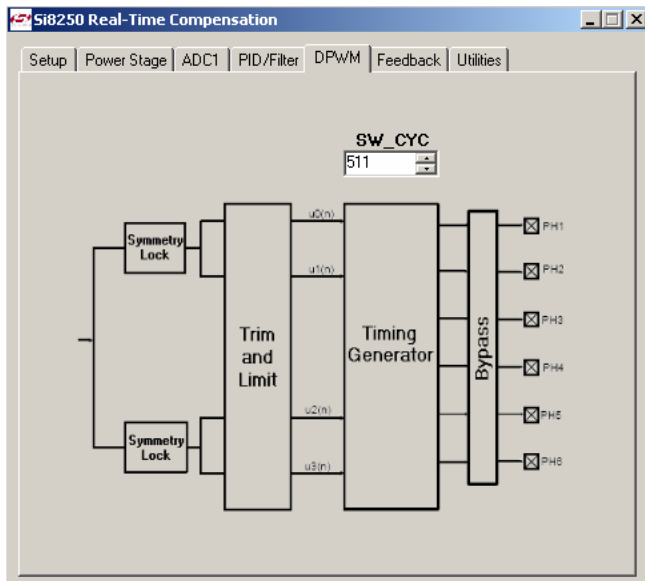


Figure 15. DPWM GUI

 


Figure 16. Feedback GUI

The default system configuration is used in the Setup GUI of Figure 11. The values in Figure 12 are given except for the load value, which is calculated by dividing the nominal output voltage by the full load current (i.e., 3.3 V/ 20 A).

ADC1 setup (Figure 13) uses a 4 mV LSB size to avoid limit cycling yet provide adequate measurement sensitivity (for more information, please see Application Note “AN259: Designing with the Si8250 Digital Power Controller”). The required 35 kHz bandwidth can be met using the lower speed (5 Mhz) clock setting, and provides better pole/zero control resolution for nonlinear control applications (“Appendix—Single-phase POL Reference Design Specifications” on page 17 provides an overview of nonlinear control). A calculated ADC1 sampling frequency value of 4.9 MHz (Figure 13) is calculated by multiplying the 24.5 MHz Si825x master clock frequency and PLL multiplication factor, then dividing by the ADC1 clock divider ratio (i.e.  $24.5 \times 10^6 \times 8/40$ ). The default settings for the PID/Filter (Figure 14) are maintained; it is these settings that will be modified later to achieve the desired frequency response.


Referring to the DPWM GUI of Figure 15, the SW\_CYC value determines the number of discrete DPWM time steps per switching cycle. Substituting the internal 200 MHz DPWM clock frequency (FDPWM), and the 380 Khz PWM frequency value into Equation 1 results in a value of 526; the default SW\_CYC parameter value of 511 is therefore maintained.

$$F_{\text{switch}} = \frac{F_{\text{DPWM}}}{\text{SW\_CYC}[8:0] \div 1}$$

**Equation 1. DPWM Switching Frequency**

The Feedback GUI parameters (Figure 16) are left at their default values as these parameters match the reference design hardware.

As shown in Figure 17, the values programmed into the FCS for this exercise result in a loop bandwidth of 11,283 Hz with a phase margin (PM) of 38.58 degrees. The parameters in the PID/Filter GUI will be adjusted to achieve the target response of 35 KHz and 45 degrees phase margin.

 

**Figure 17. Power Stage Effects**

## 5.2. Filter Coefficients



As configured for this design, the Si825x DSP filter engine has a first-stage PID filter, followed by a second stage two-pole low pass filter (LPF). The PID filter has three coefficients:  $k_p$ ,  $k_i$ , and  $k_d$ . For more information on the operation of these parameters, please see Application Note "AN259: Designing with the Si825x Digital Power Controller". A short summary of the changes in frequency response with changes in coefficient values is as follows:

- Increasing  $k_i$  provides more low frequency loop gain but less phase margin.
- Increasing  $k_d$  provides more high frequency, greater loop bandwidth and more phase margin, but increases output voltage noise.
- Increasing  $k_p$  provides higher loop gain.

The LPF provides two poles and an adjustable output gain. Poles  $a_1$ ,  $a_2$  set the corner frequencies of the LPF. These poles reduce switching noise and help optimize phase margin and loop bandwidth values. Increasing  $a_3$  increases loop gain and typically increases phase margin.

## 5.3. Adjusting Frequency Response

The results of Figure 17 show both loop gain and phase margin below the target values. Increasing loop gain by increasing the value of  $a_3$  will improve both. With  $a_3$  now adjusted to 0x66, as shown in Figure 18, the bandwidth increases to 35,250 KHz and phase margin increases to 49.95 degrees.

 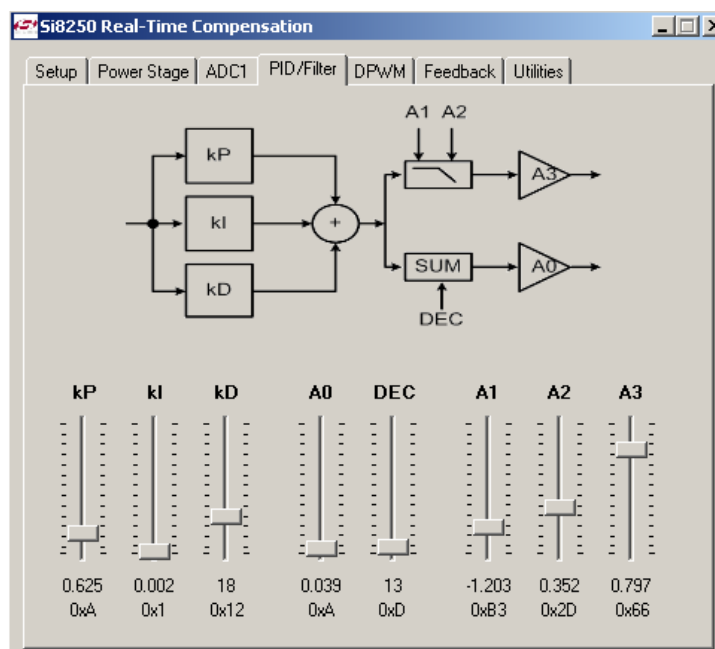

**Figure 18. Final Filter Compensation Settings**

Although Figure 18 shows the frequency response for the entire closed-loop system, other aspects of the simulation can be observed separately. For example, the open-loop frequency response of just the PID filter can be observed by simply "unchecking" the other system blocks as shown in Figure 19. The resulting response of only the PID filter is shown in Figure 20.

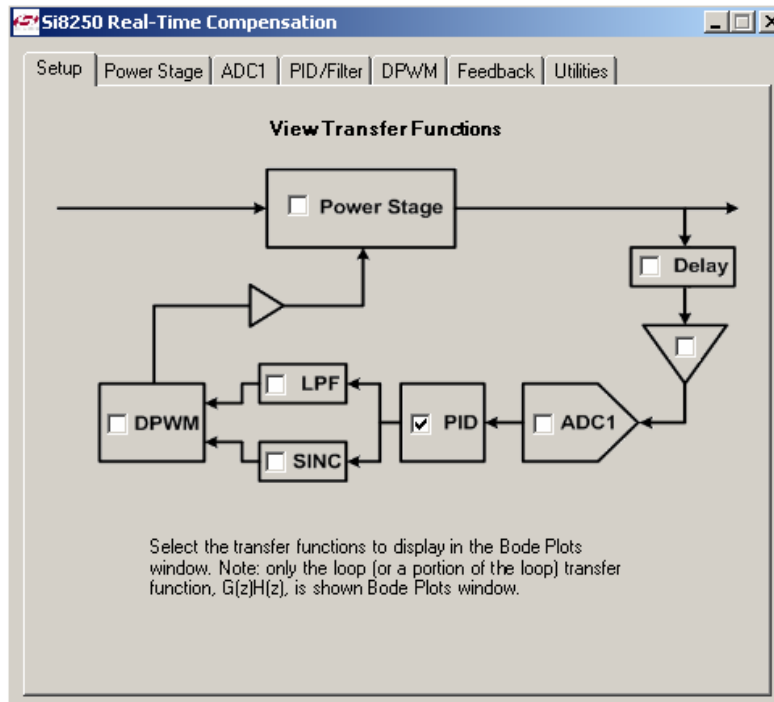


Figure 19. Observing PID Filter Response

 


Figure 20. PID Filter Response




## APPENDIX—SINGLE-PHASE POL REFERENCE DESIGN SPECIFICATIONS

### Introduction

The specifications below summarize the Si825x Single-phase POL Reference Design.

- Input voltage: 10–15 V<sub>DC</sub>
- Output voltage: 3.3 V<sub>DC</sub> @ 20 A max
- Switching frequency: 380 kHz ±2%
- Output inductor: 1 μH ±20% (DCR: 1.56 mΩ)
- Output caps: 410 μF ±20% (Capacitor ESR: 1.25 mΩ)
- RDS(on): 2.5 mΩ
- Steady-State Bandwidth: ~35 kHz
- Steady-State Phase margin: ~ 45 deg
- Transient BW: ~100 kHz
- Transient PM: ~40 deg
- Power efficiency: up to 92%
- Line Regulation: 0.42% (15 A load)
- Load Regulation: 0.3% (0~18 A load)
- Transient Response:
  - 100 mv under/overshoot
  - 20 us recovery time
  - 5–10 A, 2.5 A/μs

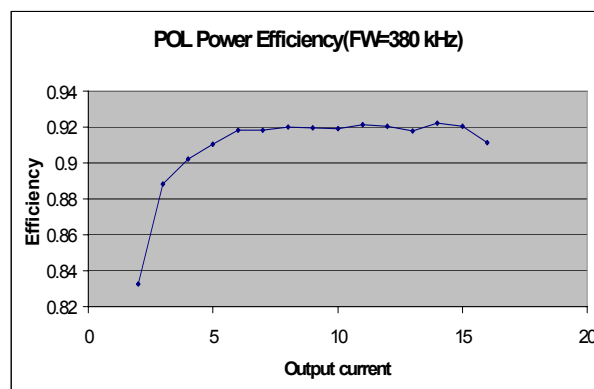


**Figure 21. Power Efficiency Curve with Load Changing**

**Note:** Under load and over temperature, the output capacitors typically lose 20 percent of their rated value. Therefore, the nominal 410 μF output caps modeled here can easily drop to 328 μF or less. The FCS can be used to simulate these and various other effects.

## Non-Linear Control

The measured loop frequency response of the Si825x Single-phase POL Reference Design is shown in Figure 22.

 

**Figure 22. POL Loop Frequency Response Measured with Network Analyzer (12 V Input Voltage at 8 A)**

Different filter coefficients are brought into play during system operation, depending on load conditions. The "steady-state" PID coefficients for the Si825x Single-phase POL reference design are  $k_p = 0x0B$ ,  $k_i = 0x01$ ,  $k_d = 0x18$ ,  $a_1 = 0xB3$ ,  $a_2 = 0x2E$ ,  $a_3 = 0x28$ .

A set of "transient response" (nonlinear control) coefficients are automatically enabled at the onset of a load transient. Figure 23 illustrates the algorithm executed by the POL to quickly resolve a transient (for more information, please see "AN271: Si8250 Real-time Kernel Overview"). Figure 24 shows the response improvement delivered by nonlinear control.

 


Figure 23. Non linear Control Kernel Algorithm

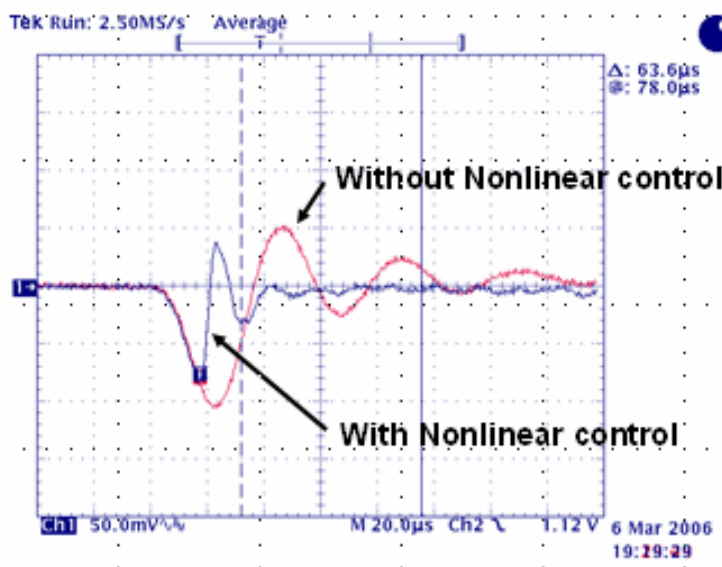


Figure 24. Transient Response with Load Step from 25% to 50%, di/dt 2.5 A/us

## RELEVANT DOCUMENTS

- Si825x Data Sheet
- Si825x Users Manual
- Application Note 259: "Designing with the Si8250 Digital Power Controller"
- Application Note 271: "Si8250 Real-time Kernel Overview"

NOTES:

## CONTACT INFORMATION

Silicon Laboratories Inc.  
4635 Boston Lane  
Austin, TX 78735  
Tel: 1+(512) 416-8500  
Fax: 1+(512) 416-9669  
Toll Free: 1+(877) 444-3032  
Email: [powerproducts@silabs.com](mailto:powerproducts@silabs.com)  
Internet: [www.silabs.com](http://www.silabs.com)

The information in this document is believed to be accurate in all respects at the time of publication but is subject to change without notice. Silicon Laboratories assumes no responsibility for errors and omissions, and disclaims responsibility for any consequences resulting from the use of information included herein. Additionally, Silicon Laboratories assumes no responsibility for the functioning of undescribed features or parameters. Silicon Laboratories reserves the right to make changes without further notice. Silicon Laboratories makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does Silicon Laboratories assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation consequential or incidental damages. Silicon Laboratories products are not designed, intended, or authorized for use in applications intended to support or sustain life, or for any other application in which the failure of the Silicon Laboratories product could create a situation where personal injury or death may occur. Should Buyer purchase or use Silicon Laboratories products for any such unintended or unauthorized application, Buyer shall indemnify and hold Silicon Laboratories harmless against all claims and damages.

Silicon Laboratories and Silicon Labs are trademarks of Silicon Laboratories Inc.

Other products or brandnames mentioned herein are trademarks or registered trademarks of their respective holders.